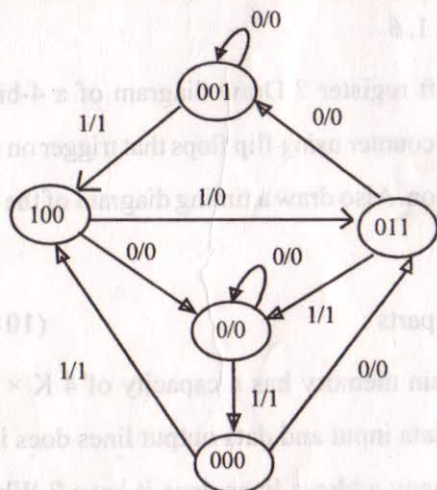


5. Answer any two parts :

(10× 20)

(a) A sequential circuit has one input and one output. The state diagram is shown in following figure :



Design the sequential circuit with T flip-flops.

(b) A sequential circuit has four flip-flops A, B, C, D and an input x. It is described by following state equations :

$$A(t+1) = (C D' + C' D) x + (C D + C' D') x'$$

$$B(t+1) = A$$

$$C(t+1) = B$$

$$D(t+1) = C.$$

(i) Obtain the sequence of states when  $x = 1$  starting from  $ABCD = 0001$ .

(ii) Obtain the sequence of states when  $x = 0$  starting from  $ABCD = 0000$ .

(c) Write short notes on any two of the following :

(i) Asynchronous sequential logic versus Synchronous sequential logic.

(ii) Hazards in combinational and sequential circuits.

(iii) State reduction in sequential circuits.

Printed Pa 4

ECS3

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0109

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. III) THEORY EXAMINATION 2011-12

DIGITAL LOGIC DESIGN

Time : 3 Hours

Total Marks : 100

Note :- Answer all questions.

1. Answer any four parts :

(5×4=20)

(a) How can functionalities of the OR gate be realized using only NAND gates ?

(b) Simplify following boolean expressions :

(i)  $A + A'B + A'B'C + A'B'C'D + A'B'C'D'E + A'B'C'D'E'F$

(ii)  $D(A'+B) + B'(C+AD)$

(c) What is Hamming Code ? How it is used for detecting and correcting errors ? Explain with the help of suitable example.

(d) Express the following boolean function F in a sum of minterms and a product of maxterms :

$$F(x, y, z) = (xy + z)(y + xz)$$

(e) Simplify the boolean function G using the don't care conditions d using Karnaugh map :

$$G = A'B'D + A'CD + A'BC$$

$$d = A'BC'D + ACD + A'B'D'$$

(f) (i) Convert the decimal number 25.2 to binary number.

(ii) Perform following arithmetic operation in binary using signed 2' complement representation :

$$(-42) - (-13)$$

2. Answer any **four** parts : (5×4=20)

(a) Design a logic circuit whose output is 1 only when a majority of inputs A, B, C are 0.

(b) Implement a full subtractor with two half subtractors and an OR gate.

(c) Implement the following boolean function F using three half adder circuits :

$$F(A, B, C) = A \oplus B \oplus C.$$

(d) Design a combinational circuit that compares the magnitude of two 4 bit numbers and its output indicates whether  $A > B$ ,  $A = B$  or  $A < B$ .

(e) What is multiplexer ? Give implementation of a full adder circuit using 4×1 multiplexers.

(f) What is priority encoder ? Explain with the help of suitable example.

3. Answer any **two** parts : (10×2=20)

(a) (i) What is flip-flop ? Draw the logic diagram and give the characteristic table of J K flip-flop.

(ii) Explain the race condition in context of RS flip-flop.

(v) Design a binary counter using J K flip-flops having the following repeated sequences :

0, 4, 2, 1, 6

(c) What is shift register ? Draw diagram of a 4-bit binary ripple down counter using flip flops that trigger on negative edge transition. Also draw a timing diagram of the counter.

4. Answer any **two** parts : (10×2=20)

(a) (i) A certain memory has a capacity of  $4 K \times 8$ . How many data input and data output lines does it have ? How many address lines does it have ? What is its capacity in Bytes ?

(ii) Discuss the following types of ROM, PROM, EPROM, EEPROM.

(b) (i) Design a  $16 \times 8$  memory using  $16 \times 4$  memory units.

(ii) Differentiate between programmable array logic (PAL) and programmable logic arrays (PLA).

(c) (i) Draw the logic diagram of 4 input multiplexer. Further show how 4-input multiplexer can be realized using 2-input multiplexers.

(ii) Draw the logic diagram of one line to 8-line demultiplexer.