

(b) What is the basic architecture of a PLA ? How is the capacity of a PLA specified ? How is it programmed ? Explain.

(c) Draw the logic configuration of four input and four output PAL and explain.

5. Attempt any two parts of the following : (10×2=20)

(a) Differentiate between asynchronous and synchronous sequential circuit. Define fundamental mode of operation.

(b) Define critical race and non-critical race. Discuss the concept of non critical race with examples.

(c) Describe briefly the excitation table and output table of a fundamental mode asynchronous sequential circuit.

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0323

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. III) THEORY EXAMINATION 2011-12

DIGITAL ELECTRONICS

Time : 3 Hours

Total Marks : 100

Note :- Attempt all questions. Each question carries equal marks.

1. Attempt any four parts of the following : (5×4=20)

(a) Represent decimal number “-13” in all four methods of negative binary number representation using eight bits.

(b) Perform the following subtraction using 2's complement method :

(i) 01000-01001

(ii) 0011.1001-0001.1110

(c) Add the following numbers :

(i) $(ABC)_{16} + (CDE)_{16}$

(ii) $(77)_8 + (107)_8$

(d) Detect and correct error (if any) in the following received even parity Hamming code word 00111101010. Also find out the correct message.

(e) Minimize the given Boolean function using K-Map and implement the simplified function using NAND gates only.

$$F(A, B, C, D) = \sum m(0, 1, 2, 9, 11, 15) + d(8, 10, 14).$$

(f) Minimize the following function using Quine Mc Clusky method:

$$f(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 9, 10, 13)$$

2. Attempt any **two** parts of the following : (10×2=20)

(a) Construct a BCD to excess 3 code converter with a 4 bit adder. What must be done to change the circuit to an excess 3 to BCD code converter ?

(b) What is magnitude comparator ? Design a three bit comparator circuit using logic gates.

(c) (i) Design a full subtractor circuit with a decoder and two OR gates.

(ii) Implement the function :


$$F(A, B, C) = \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} C + A B C$$

using 4 : 1 multiplexer using A and B variables to the selection lines.

3. Attempt any **two** parts of the following : (10×2=20)

(a) Draw RS flip-flop and write the characteristic table and characteristic equation for it. Explain how will you convert it into D flip-flop.

 (b) Design a circuit that implements the state diagram.



(c) Design a synchronous counter using J-K flip-flop for the following input sequences :

A	B	C
0	0	0
0	0	1
0	1	0
1	0	0
1	0	1
1	1	0
0	0	0

4. Attempt any **two** parts of the following : (10×2=20)

(a) What is ROM ? What are the various types of ROM ? Explain.