

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0325

Roll No.

--	--	--	--	--	--	--	--	--	--	--

**B. Tech.**

(SEM. III) ODD SEMESTER THEORY

EXAMINATION 2013-14

## FUNDAMENTALS OF NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours

Total Marks : 100

Note : Attempt all questions.

1. Attempt any four parts :

(5×4=20)

(a) Define the signal, also explain different types of standard signals with proper figure.

(b) Consider a system S with input  $x[n]$  and output  $y[n]$  related by:

$$y[n] = x[n] \{g[n] + g[n-1]\},$$

(i) If  $g[n] = 1$ , for all  $n$ , show that S is time invariant.

(ii) If  $g[n] = n$ , show that S is not time invariant.

- (c) For the network shown, write the mess equation in terms of (i) Differential equation and (ii) the complex frequency variables.

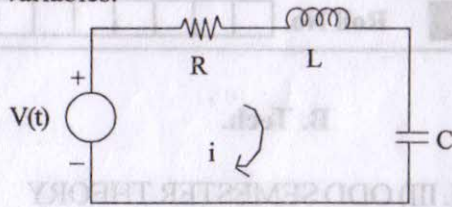


Fig. 1

- (d) If the system function of a network is given as :

$$H(s) = \frac{1}{(s+2)(s+3)}, \text{ find the response } R(s), \text{ if the}$$

excitation is unit step signal.

- (e) Prove that (i)  $\delta(x) = -\delta(-x)$ , (ii)  $-\delta(x) = x\delta(x)$ , where  $\delta(x)$  is impulse function.

2. Attempt any four parts : (5×4=20)

- (a) The port currents of a two port network are given by :

$$I_1 = 2.5V_1 - V_2$$

$$I_2 = -V_1 + 5V_2$$

Find equivalent  $\pi$  network.

- (b) Derive the condition of reciprocity for ABCD-parameters.

- (c) The transform of current is  $I(s) = \frac{2s}{(s+1)(s+2)}$ . Sketch

its pole-zero plot and obtain time domain response  $i(t)$ . Also write a short note on significance of the network transfer function.

- (d) Using Thevenin's theorem, find the current through load impedance  $Z_L$  shown in the Fig. 2.

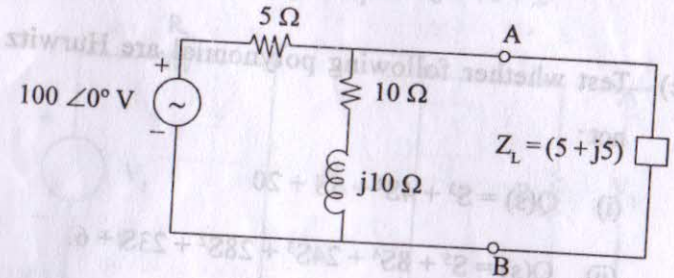


Fig. 2

- (e) Using the initial and final value theorems find  $f(0+)$  and  $f(\infty)$  for the following :

(i)  $F(s) = \frac{(s+1)(s+2)}{(s+3)(s+4)}$

(ii)  $F(s) = \frac{s^2 + 2s + 3}{s(s+1)(s+4)}$

3. Attempt any four parts : (5×4=20)

- (a) Discuss why the following functions are not positive real function :

(i)  $\frac{s^2 + 2s + 1}{s^2}$

(ii)  $\frac{(s^2 + 1)(s^2 + 2)}{s(s^2 + 3)}$

(b) Given the admittance function :

$$Y(s) = \frac{H_0(s^2 + b_1s + b_0)}{s^2 + a_1s + a_0}$$

(c) Test whether following polynomial are Hurwitz or not :

(i)  $Q(s) = S^3 + 4S^2 + 5S + 20$

(ii)  $Q(s) = S^5 + 8S^4 + 24S^3 + 28S^2 + 23S + 6.$

(d) Determine Foster I form of following driving point impedance function :

$$Z(s) = \frac{(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

(e) Write the properties of LC driving point Imittance function.

4. Attempt any two parts : (10×2=20)

(a) Discuss the properties of transfer functions, also find the residue condition for the following circuit :

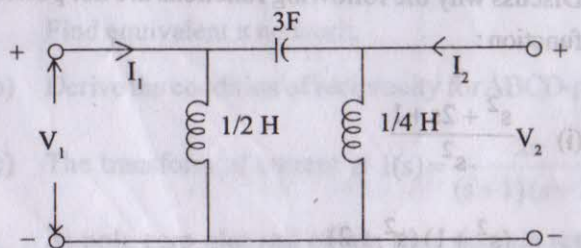


Fig. 3

(b) Synthesize  $N_a$  with termination resistors  $R_2 = 4$  ohm,

$R_1 = 1$  ohm to give  $\frac{V_2}{V_1} = \frac{12s^2}{15s^2 + 7s + 2}$

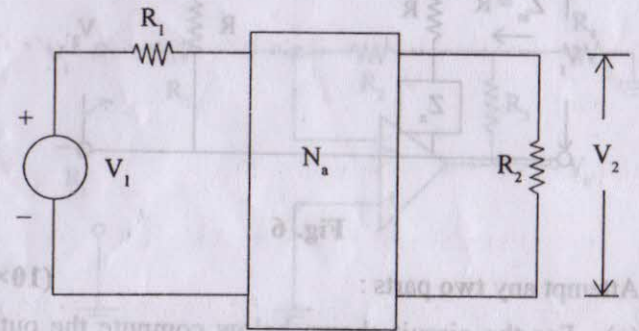


Fig. 4

(c) For the network shown in Fig. 5, 6 below, find the voltage ratio transfer functions  $V_2/V_1$ .

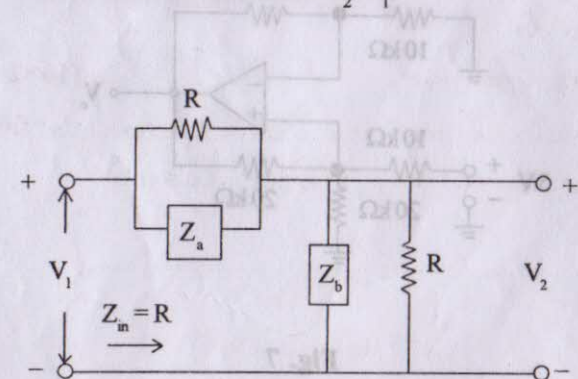


Fig. 5

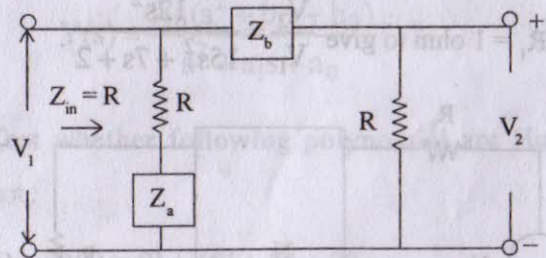


Fig. 6

5. Attempt any two parts : (10×2=20)

- (a) For the circuit shown below compute the output  $V_o$ . Also determine the input resistance  $R_i$  as seen by the source.

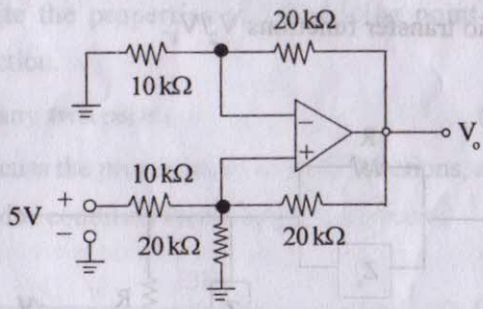


Fig. 7

- (b) Compute the gain  $V_o/V_i$  for the Op-Amp circuit given below. Also find the input resistance  $R_i$ .

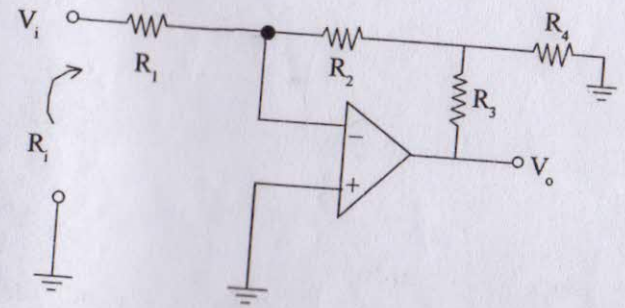


Fig. 8

- (c) Design the low pass and high pass active filters using Op-Amp.