

Fig. 4(a)

- (b) Enlist the properties of transfer function of a network. Obtain the zero of transmission of

$$\text{the function } Z(s) = \frac{(s+1)(s+4)}{(s+2)(s+3)}$$

- (c) Explain the term "zeros of transmission". Realize the network function

$$Y_{21}(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)} \text{ with } 1\Omega$$

termination.

5 Answer any two parts of the following :  $10 \times 2 = 20$

- (a) A function is given by  $Z(s) = \frac{s^4 + 7s^2 + 9}{s(s^2 + 4)}$

as active LC network.

- (b) Find the inverse transform of

$$F(s) = \frac{1}{(s^2 + a^2)^2} \text{ using convolution integral.}$$

- (c) Calculate the current flowing through the branch containing resistance  $R_1$  of Fig. 5(c) using Thevenin's theorem.

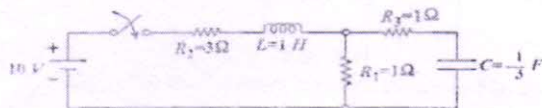


Fig. 5(c)



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0325

Roll No.

B.Tech

(SEM III) ODD SEMESTER THEORY EXAMINATION 2009-10  
FUNDAMENTALS OF NETWORK ANALYSIS & SYNTHESIS

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all five questions. All questions carry equal marks. Assume missing data if any.

- 1 Attempt any four parts of the following :

5×4=20

- (a) With the help of mathematical expressions and characteristics curves, explain unit step, impulse and ramp signals used to analyse the network.  
(b) Synthesize the waveform as shown in Fig. 1(b).


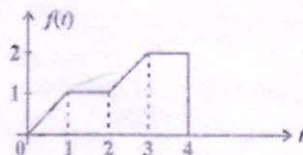


Fig. 1(b)

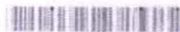- (c) Explain the exponential function with suitable expression and curves.  
(d) Show that the derivative of a parabolic function is a ramp function and derivative of ramp function is a step function.



- (e) Discuss the concept of initial and final conditions in network analysis with suitable example.
- (f) Find the current  $i(t)$  in a series  $R-L-C$  circuit comprising  $R = 3\Omega$ ,  $L = 1H$  and  $C = 0.5 F$  when ramp voltage 12 volts is applied.

2 Attempt any three parts of the following :  $6 \frac{2}{3} \times 3 = 20$

- (a) Define initial value theorem and final value theorem. Also find initial and final values of

$$\text{the function : } F(s) = \frac{s^3 + 3s^2 + 3s + 1}{s^2 + 2s + 2}$$

- (b) Determine the impulse response of transfer function

$$G(s) = \frac{s^2 + 3}{s(s+4)(s^2 + 4)}$$
 of a system.

- (c) Find the driving point impedance function of the network shown in Fig. 2(c). Also plot the poles and zeros of  $z(s)$  on s-plane.

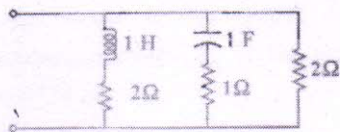


Fig. 2(c)

- (d) For the two-port network shown in Fig. 2(d). Determine the admittance matrix :

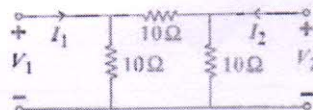


Fig. 2(d)

- (e) Prove that in a parallel-parallel interconnected two networks with admittance matrix  $[Y_A]$  and  $[Y_B]$  respectively, the overall Y-matrix is given as  $[Y] = [Y_A] + [Y_B]$ .

3 Answer any two parts of the following :  $10 \times 2 = 20$

- (a) What is a positive real function ? Also check whether the function

$$Z(s) = \frac{2s^2 + 3s + 1}{s^3 + 3s^2 + s + 2}$$
 is a positive real function or not.

- (b) Enlist the properties of RL admittance function. Check whether the function

$$Z(s) = \frac{(s^2 + 1)(s^2 + 4)}{s(s^2 + 2)}$$
 is RL network or not.

- (c) Realize the following LC impedance function as (i) Foster-II form (ii) Cauer-I form

$$Z_{LC}(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$

4 Answer any two parts of the following :  $10 \times 2 = 20$

- (a) Find the transfer function of the network shown in Fig. 4(a). Also sketch pole-zero configuration of the network.