

(Following Paper ID and Roll No. to be filled in your Answer Book)

Paper ID :131312

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. III) THEORY EXAMINATION, 2015-16

DIGITAL DESIGN

[Time : 3 hours]

[Total Marks : 100]

SECTION - A

1. Attempt **all** parts. All parts carry **equal** marks. Write answer of each part in short. (2x10=20)
 - (a) Perform the Subtraction using 2's complement 23-46.
 - (b) Simplify the following Boolean expression:
$$(AB + AC)' + A'B'C$$
 - (c) Design a Half Adder using NAND gates only.
 - (d) How many flip flops are required to design a Mod 59 Binary Counter.
 - (e) Differentiate between Synchronous and Asynchronous sequential circuits.

- (f) Construct basic SRAM memory Cell.
- (g) How many address lines and data input/ output lines are required for a 64K X 12 memory?
- (h) Design a Half Adder using Multiplexer.
- (i) Design a divide by 4 Asynchronous counter using JK Flip Flop.
- (j) How many Flip Flops are required for Mod-10 counter?

SECTION - B

Attempt **any five** questions from this section. (10x5=50)

2. Minimize the following using Tabular method:

$$f(A,B,C,D) = \sum m(4, 5, 6, 8, 9, 10, 13) + \sum d(0, 7, 15)$$

- 3. Obtain Hamming codeword for the given data: "11001001010". Use even parity.
- 4. Convert the decimal number 42.50 in Octal, Hexadecimal, Gray, 8421, Excess-3.
- 5. Design a 4-bit by 4-bit Binary Multiplier.
- 6. Realize the following expression using 8:1 Multiplexer:
 $F(A,B,C,D) = A'BC + B'C'D + A'C'$

- 7. Design a 3-bit binary to Gray Code converter using PLA.
- 8. Draw and explain 4-bit Universal shift Register.
- 9. Design a 3-bit UP-DOWN counter.

SECTION - C

Attempt **any two** questions from this section. (15X2=30)

- 10. Obtain the reduced flow table for an Asynchronous sequential circuit that has two inputs x_2 and x_1 and one output z . When $x_1=0$, the output $z=0$. The first change in x_2 that occurs while $x_1=1$ will cause output z to be 1. The output z will remain 1 until x_1 returns to zero.
- 11. Design a Sequence Generator to generate the given sequence: "10100011".
- 12. Design a circuit for addition BCD numbers.

—x—