

Section-C

Attempt **any two** questions from this section. $15 \times 2 = 30$

10. (a) Implement the following Boolean function with a multiplexer:

$$F(A, B, C, D) = \sum (0, 2, 5, 7, 11, 14)$$

- (b) Using a decoder and external gates, design the combinational circuit defined by the following three Boolean functions:

$$F1 = (y' + x)z$$

$$F2 = y'z' + yz'$$

$$F3 = (x' + y)z$$

11. Minimize the following Boolean function using tabular method (Quine Mc-Cluskey method)

$$f(A, B, C, D) \sum = m(4, 5, 6, 8, 9, 10, 13) + \sum d(0, 7, 15)$$

12. A sequential circuit has two JK flip-flops A and B, two inputs X and Y, and one output Z. The flip-flop input equations are:

$$JA = BX + B'Y' \quad KA = B'XY'$$

$$JB = A'X \quad KB = A + XY'$$

$$Z = AXY + BX'Y'$$

- Draw the logic diagram
- Derive the state equations.
- Obtain the state table, state diagram.

—x—

(Following Paper ID and Roll No. to be filled in your Answer Book)

Paper ID : 131305

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. III) THEORY EXAMINATION, 2015-16 DIGITAL LOGIC DESIGN

[Time: 3 hours]

[Total Marks: 100]

Section-A

1. Attempt **all** parts. All parts carry equal marks. Write answer of each part in short. (10 × 2 = 20)
- Define Primitive Flow table.
 - What is race around condition in JK flip flop?
 - How many address lines and input output lines are needed in 2G X 8 memory unit.
 - Differentiate between EPROM and EEPROM.
 - Design full adder using two half adders.

- (f) Differentiate between encoders and decoders.
- (g) Subtract 11010 from 10110 using 2's complement.
- (h) Represent $(213.25)_{10}$ in single precision floating point representation.
- (i) Convert decimal 9 into gray code.
- (j) Simplify the Boolean expression: $Y=(A+B)(A+C')(B'+C')$.

Section-B

Attempt **any five** questions from this section. (10×5=50)

- 2. Obtain Hamming codeword for the given data: "11001001010"
- 3. Design a 4-bit by 4-bit Binary Multiplier.
- 4. Design a 3-bit binary to Gray Code converter using PLA.
- 5. Explain the difference between SRAM and DRAM.
- 6. Draw and explain 4-bit Universal shift Register.

- 7. Design a clocked sequential circuit that operates according to the state diagram shown:

 


Figure: State Diagram

Implement the circuit using D Flip-Flop.

- 8. Describe the general procedures that must be followed to ensure a race-free state assignment with example.
- 9. Obtain the reduced flow table for an Asynchronous sequential circuit that has two inputs x_2 and x_1 and one output z . When $x_1=0$ the output $z=0$. The first change in x_2 that occurs while $x_1=1$ will cause output z to be 1. The output z will remain 1 until x_1 returns to zero.