

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 131307

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. III) (ODD SEM.) THEORY
EXAMINATION, 2014-15

FUNDAMENTALS OF NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all questions.

1 Attempt any four parts : 5×4=20

(a) Evaluate the value of

$$\int_{-3}^4 \delta(t-4)(t^2 + 2t + 3)dt$$

(b) If the response of a time-invariant system $h(t)$

is $e^{-t}u(t)$ then determine the response due to
excitation of

$$e(t) = 2\delta(t-1) + 3\delta(t-4) - 3\delta(t+1).$$

(c) Define the following terms :

- (i) Network Analysis
- (ii) Network Synthesis
- (iii) Complex Frequency.

(d) If initial conditions are $x(0^+) = +1$ and

$x'(0^+) = -1$ then determine the value of

$$x'(t) + 4x'(t) + 3x(t) = 0.$$

(e) Describe the following signals :

- (i) Unit Step
- (ii) Exponential
- (iii) Ramp Signal
- (iv) Unit Impulse.

2 Attempt any **four** parts :

5×4=20

(a) Find the initial and final value of the function

$$x(s) = \frac{(s+1)(s+4)}{s(s+2)(s+3)}$$

131307]

2

[Contd... 131307]

(b) Find current in 4Ω resistance of Fig. 1 using Thevenin theorem.

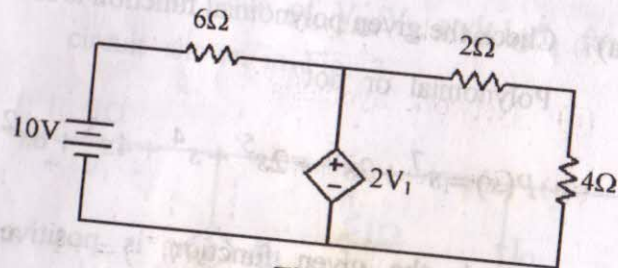


Fig. 1

(c) Determine the Y parameters of the network shown in Fig. 2.

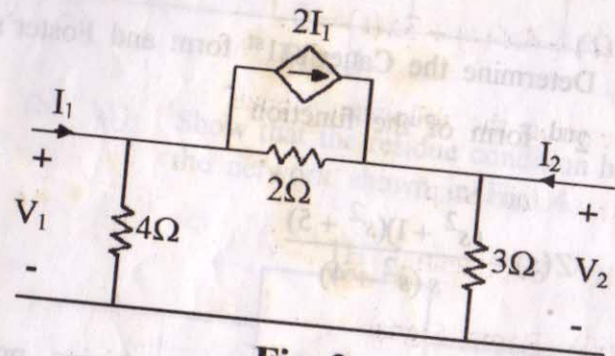


Fig. 2

(d) Represent Y-parameters in terms of h-parameters.

(e) Find the inverse Laplace transform of

$$X(s) = \frac{s}{(s+1)((s+2)^2+1)}$$

3

[Contd...

3 Attempt any **four** parts : $5 \times 4 = 20$

(a) Check the given polynomial function is Hurwitz

Polynomial or not?

$$P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4.$$

(b) Check the given function is positive real

function or not? $f(s) = \frac{(s+1)(s+4)}{(s+2)(s+3)}$

(c) Determine the Cauer's 1st form and Foster's 2nd form of the function

$$Z(s) = \frac{(s^2 + 1)(s^2 + 5)}{s(s^2 + 4)}$$

(d) Write the properties of RL driving point impedance.

(e) Draw the Cauer's 2nd form of the function

$$Z(s) = \frac{s(s+3)}{(s+1)(s+5)}$$

4 Attempt any **two** parts :

(a) Find the value of V_O/V_1 and I_O/I_1 for the circuit shown in Fig. 3.

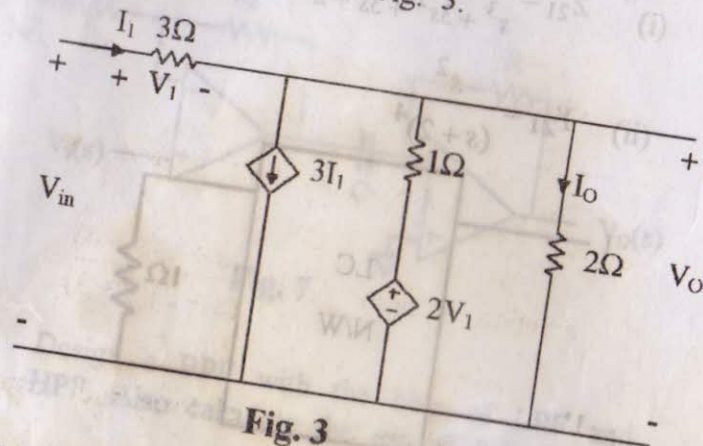


Fig. 3

(b) (i) Show that the residue condition hold for the network shown in Fig. 4.

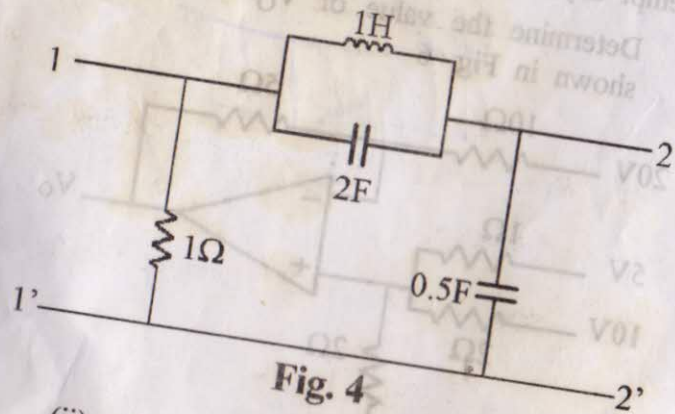


Fig. 4

(ii) Draw the circuit of a network that has multiple poles on the $j\omega$ axis.

(c) Synthesize the following terms into the term shown in Fig. 5.

(i) $Z_{21} = \frac{1}{s^3 + 3s^2 + 3s + 2}$

(ii) $Y_{21} = \frac{s^2}{(s+2)^4}$



Fig. 5

5 Attempt any two parts: 10×2=20

(a) Determine the value of V_O for the circuit shown in Fig. 6

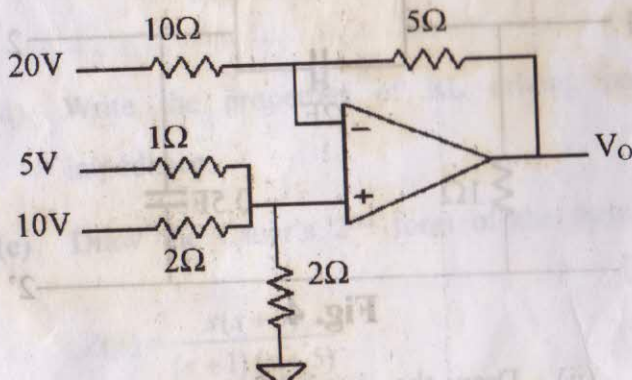


Fig. 6

(b) Determine the value $\frac{V_O(s)}{V_i(s)}$ for the circuit shown in Fig. 7.

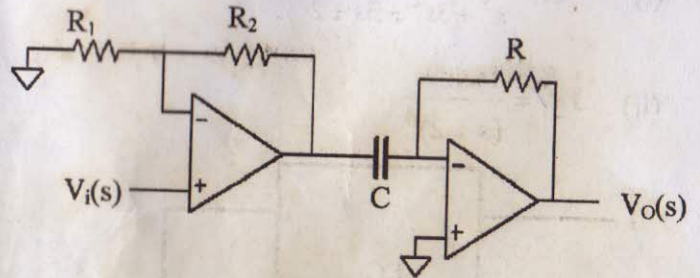


Fig. 7

(c) Design a BPF with the help of LPF and HPF. Also calculate the cut-off frequency.

